

ETEC 1120 Formula Sheet

General

$$\% \text{ error} = \frac{|\text{measured} - \text{calculated}|}{\text{measured}} \times 100 \quad R = \frac{V}{I} \quad I = \frac{V}{R} \quad V = IR$$

The Practical Diode

$$V_R = V_S - 0.7V \quad I_T = \frac{V_S - 0.7V}{R_1} \quad I_{F(\max)} = \frac{P_{D(\max)}}{V_F}$$

The Complete Diode

$$V_F = 0.7V + I_F R_B \quad P_D = V_F I_F \quad \text{Reverse Current} \\ I_R = I_S + I_{SL}$$

The Zener Diode

$$Z_Z = \frac{\Delta V_Z}{\Delta I_Z} \quad \left| \Delta V_Z = \text{the change in } V_Z \right. \quad I_{ZM} = \frac{P_{D(\max)}}{V_Z}$$

Transformers

$$V_2 = \frac{N_2}{N_1} V_1 \quad I_2 = \frac{N_2}{N_1} I_1 \quad I_2 = \frac{V_1}{V_2} I_1 \quad V_{(pk)} = \frac{V_{\text{rms}}}{0.707}$$

Rectifiers (Half Wave)

$$V_{L(pk)} = V_{2(pk)} - 0.7V \quad I_{L(pk)} = \frac{V_{L(pk)}}{R_L} \quad V_{\text{ave}} = 0.318 V_{L(pk)} \quad \text{PIV} = V_{2(pk)} \text{ (no filter)}$$
$$V_{2(pk)} = \frac{N_2}{N_1} V_{1(pk)} \quad V_{\text{ave}} = \frac{V_{L(pk)}}{\pi} \quad I_{\text{ave}} = 0.318 I_{L(pk)} \quad f_{\text{out}} = f_{\text{in}} \quad I_{\text{ave}} = \frac{V_{\text{ave}}}{R_L}$$

Rectifiers (Full Wave)

$$V_{L(pk)} = \frac{V_{2(pk)}}{2} - 0.7V \text{ (center-tapped)} \quad I_{\text{ave}} = \frac{2I_{L(pk)}}{\pi} \quad V_{\text{ave}} = 0.636 V_{L(pk)}$$
$$V_{L(pk)} = V_{2(pk)} - 1.4V \text{ (Bridge)} \quad V_{\text{ave}} = \frac{2V_{L(pk)}}{\pi} \quad I_{\text{ave}} = 0.636 I_{L(pk)}$$
$$f_{\text{out}} = 2f_{\text{in}} \quad \text{PIV} = V_{2(pk)} - 0.7V \text{ (no filter)}$$

Filter Capacitor

$$\tau = RC$$

$$T = 5(RC)$$

$$V_r = \frac{I_L}{fC}$$

$$V_r = \frac{I_L t}{C}$$

$$\text{Charge/Discharge Time} \quad C = \frac{I(t)}{\Delta V_C} \quad t = \frac{CV}{I}$$

$$I_{\text{surge}} = \frac{V_{2(pk)}}{R_W + R_B}$$

$$V_{\text{dc}} = V_{(pk)} - \frac{V_r}{2}$$

$$\text{PIV} = 2 V_{2(pk)} \text{ (half wave filtered)}$$

$$\text{PIV} = V_{2(pk)} \text{ (full wave filtered)}$$

Zener Regulator

$$I_Z = I_T - I_L$$

$$I_L = \frac{V_Z}{R_L}$$

$$R_{L(\min)} = \frac{V_Z}{I_{L(\max)}}$$

$$V_{r(\text{out})} = \frac{Z_Z \parallel R_L}{(Z_Z \parallel R_L) + R_S} V_r$$

$$I_T = \frac{V_S - V_Z}{R_S}$$