

# ELEC1120 ELECTRO PRINCIPLES I

## EXPERIMENT #2 OHM'S LAW

NAME \_\_\_\_\_

SECTION \_\_\_\_\_

### PURPOSE

To use **VOM**'s and **DMM**'s to measure the basic electrical quantities in a DC circuit and to verify Ohm's Law.

### EQUIPMENT

#### LAB SUPPLIED PARTS

DC power supply  
Triplet VOM  
Fluke DMM

#### SERIAL NUMBERS

\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

#### PARTS KIT PARTS

Resistors 1k $\Omega$  and 3.3 k $\Omega$  ¼ watt  
Set of meter leads  
Set of clip to clip jumper leads

### INTRODUCTION

Voltmeters, ammeters and ohmmeters contain many of the same parts. To save on costs a single meter that can perform all three functions is often employed. This type of meter is called a multimeter or **VOM** (Volt Ohm Milliamp meter). When this type of meter has a digital display it is often called a **DMM** (**D**igital **M**ulti**M**eter). During this lab a **VOM** and **DMM** are used to measure all three basic electrical quantities. They are also used simultaneously in a simple circuit to measure current and voltage. The data from these measurements is used to plot the linear relationship between current and voltage for a fixed resistance.

### PROCEDURE #1 VOLTAGE MEASUREMENT

- 1) Record the equipment serial numbers in the spaces provided above.
- 2) Adjust the power supply **voltage control** to minimum (fully counterclockwise) and the **current control** to maximum (fully clockwise). Set the **DMM** to measure **Volts DC** using the 2 volt range.
- 3) Connect the circuit shown in Figure 1 using the 1 k $\Omega$  resistor. Note Figure 2 shows the schematic representation of the circuit.
- 4) Turn on the power supply and **DMM**. Adjust the power supply **voltage control** so the voltage is somewhere between .450 volts and .490 volts. Note because of the small voltage it may be a little tricky to set the voltage exactly. Any value between .450 volts and .490 volts will do. **DO NOT ADJUST THE POWER SUPPLY CONTROLS FOR THE REST OF THIS PROCEDURE.**

# ELEC1120 ELECTRO PRINCIPLES I

## EXPERIMENT #2 OHM'S LAW

- 5) Change the **DMM** to the 1000 V range and record the measurement in the top row of table #1. Measurements should be recorded exactly as they appear on the **DMM** display. Change **DMM** ranges to complete the **MEASUREMENT** column of table #1. Indicate any measurement that is out of range by marking “**OR**” at the right side of table #1. Also indicate the range that gives the most accurate measurement by putting an “**\***” at the left side of the table. Do not forget to indicate the correct units.

**TABLE #1 DMM VOLTAGE MEASUREMENTS**

RANGE	MEASUREMENT
1000 V	
200 V	
20 V	
2 V	
200 mV	

- 6) Do not move the power supply controls. Replace the **DMM** with the **VOM** and record the measurements for each range in table #2 below. Indicate the range that gives the most accurate measurement by putting an “**\***” at the left side of the table.


**TABLE #2 VOM VOLTAGE MEASUREMENTS**

RANGE	MEASUREMENT
1000 V	
300 V	
100 V	
30 V	
10V	
3 V	
1 V	

# ELEC1120 ELECTRO PRINCIPLES I

## EXPERIMENT #2 OHM'S LAW

### Voltage Measurement

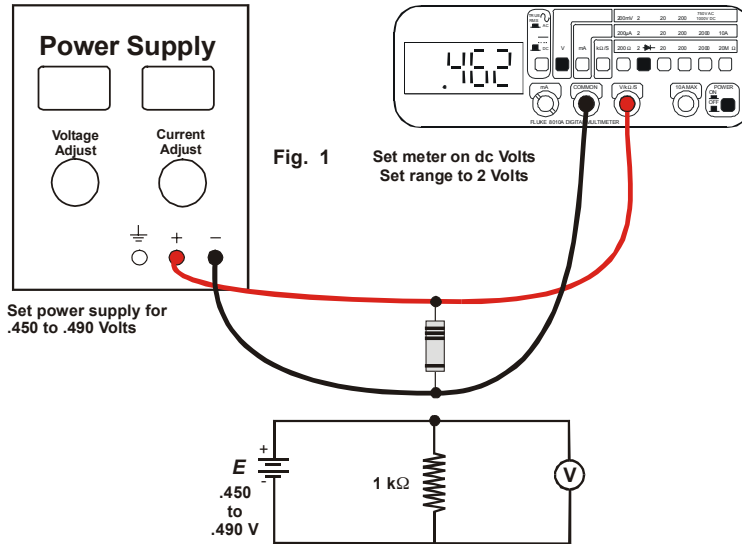

### PROCEDURE #2 CURRENT MEASUREMENT

- 1) Adjust the power supply **voltage control** to minimum (fully counterclockwise) and the **current control** to maximum (fully clockwise). Set the **DMM** to measure **Milliamps DC** on the 20 milliamp range.
- 2) Connect the circuit shown in Figure #3 using the 1 K $\Omega$  resistor. Note Figure #4 shows the schematic representation of the circuit.
- 3) Turn on the power supply and **DMM**. Adjust the power supply **voltage control** so the **DMM** indicates the current is 8.00 mA.
- 4) Set the DMM range to 2000 mA and record the measurement in row one of table #3. Measurement should be recorded exactly as they appear on the **DMM** display. Change the ranges to complete the MEASUREMENT column of table #3. Indicate any measurement that is out of range by marking “OR” at the right side of table #3. Also indicate the range that gives the most accurate measurement by putting an “\*” at the left side of table #3. Do not forget to indicate the correct units.

**TABLE #3 DMM CURRENT MEASUREMENTS**

RANGE	MEASUREMENT
2000 mA	
200 mA	
20 mA	
2 mA	
200 $\mu$ A	

# ELEC1120 ELECTRO PRINCIPLES I



## EXPERIMENT #2 OHM'S LAW

- 5) Replace the **DMM** with the **VOM** and adjust the power supply so the resistor current is 8 mA (on the 10 mA range). Enter the measurements for each DC current range in table #4 below. Indicate any measurement that is out of range by marking "OR" at the right side of the table. Also indicate the range that gives the most accurate measurement by putting an "\*" at the left side of table #4.

**TABLE #4 VOM CURRENT MEASUREMENTS**

RANGE	MEASUREMENT
1000 mA	
100 mA	
10 mA	
.1 mA	

### Current Measurement

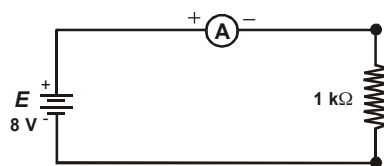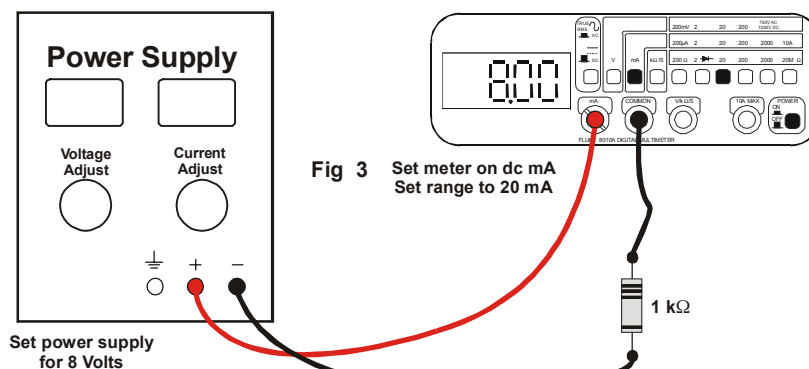

## PROCEDURE #3 RESISTANCE MEASUREMENT

- 1) Set the **DMM** to measure resistance by pressing the k $\Omega$ /S push-button and connecting the meter leads to the V/k $\Omega$ /S and COMMON terminals.
- 2) Follow the procedure described on **page 5 of the prelab** to measure and record the resistances of the 1 k $\Omega$  and 3.3 k $\Omega$  resistors.

# ELEC1120 ELECTRO PRINCIPLES I

## EXPERIMENT #2 OHM'S LAW

**TABLE #5 DMM RESISTANCE MEASUREMENTS**

RESISTOR	MEASUREMENT
1 k $\Omega$	
3.3 k $\Omega$	

- 3) Use the **VOM** to measure and record the resistances of the 1 k $\Omega$  and 3.3 k $\Omega$  resistors. Follow the procedure described on **page 3 of the prelab**.

**TABLE #6 VOM RESISTANCE MEASUREMENTS**

RESISTOR	MEASUREMENT
1 k $\Omega$	
3.3 k $\Omega$	

### **PROCEDURE #4 OHM'S LAW PLOTTING CURRENT VS VOLTAGE**

- 1) Using the **DMM** as the voltmeter and the **VOM** as the ammeter, connect the circuit shown in Figure 5. Use the 1 k $\Omega$  resistor as the resistance. Note Figure 6 shows the schematic representation of the circuit. Adjust the power supply so the resistor voltage climbs from 0 to 10 volts in 2 volt steps. In table #7 below record the **VOM**'s current level at each voltage step.

**TABLE #7 CURRENT vs VOLTAGE 1k $\Omega$**

VOLTAGE	CURRENT
0 V	
2.00 V	
4.00 V	
6.00 V	
8.00 V	
10.00 V	

# ELEC1120 ELECTRO PRINCIPLES I

## EXPERIMENT #2 OHM'S LAW

2) Replace the 1 kΩ resistor with the 3.3 kΩ resistor and complete table #8 below.

**TABLE #8 CURRENT vs VOLTAGE 3.3kΩ**

VOLTAGE	CURRENT
0 V	
2.00 V	
4.00 V	
6.00 V	
8.00 V	
10.00 V	

### Circuit for Measuring Current vs Voltage

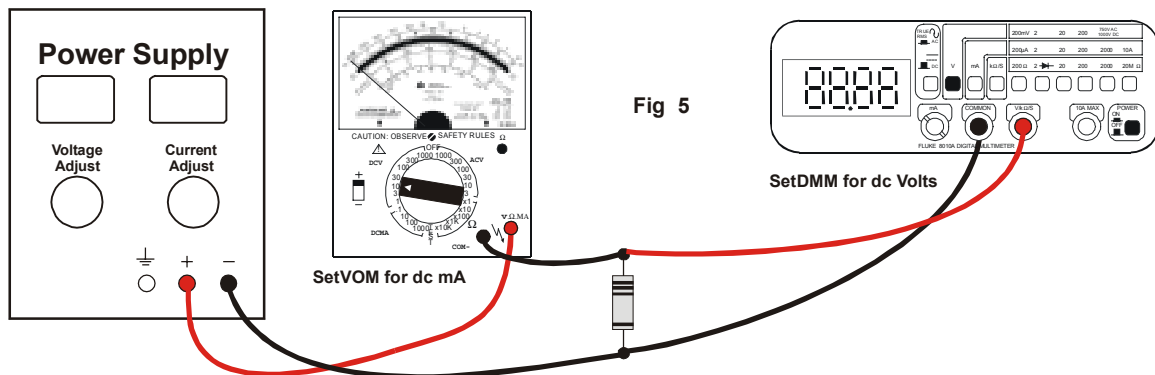


Fig 5

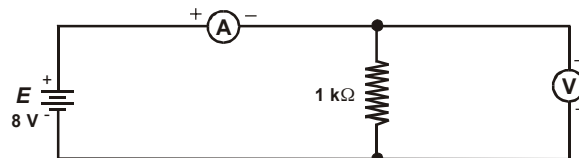


Fig. 6 Schematic Circuit for Fig 5

# ELEC1120 ELECTRO PRINCIPLES I

## EXPERIMENT #2 OHM'S LAW

- 3) Use the voltage and current values from tables #7 and #8 to plot the curves of current vs voltage for the 1 k $\Omega$  and 3.3 k $\Omega$  resistors. Clearly label each of the curves on the graph below.

### CURRENT vs VOLTAGE

